

Experiment 2

VLSI

4 Bit Carry Look Ahead Adder


Shashank Sharma

15BEE0270

L47+L48

Objective:

To design implement and test 4 Bit Carry Look Ahead Adder circuit using Xilinx ISE Tool.

 Circuit Diagram:

Design code:

```
module CLA_4bit(
    input [3:0]a,b,
    input Cin,
    output [3:0] S,
    output Cout
);
    wire [3:0]p;
    wire [3:0]g;
    wire [4:0]c;
    assign c[0]=Cin;
    assign p[0]=a[0]^b[0];
    assign g[0]=a[0]&b[0];
    assign c[1]=(p[0]&c[0])|g[0];

    assign p[1]=a[1]^b[1];
    assign g[1]= a[1]&b[1];
    assign c[2]=(p[1]&p[0]&c[0])|(p[1]&g[0])|g[1];

    assign p[2]=a[2]^b[2];
    assign g[2]=a[2]&b[2];
    assign c[3]=(p[2]&p[1]&p[0]&c[0])|(p[2]&p[1]&g[0])|(p[2]&g[1])|g[2];

    assign p[3]=a[3]^b[3];
    assign g[3]=a[3]&b[3];
    assign c[4]=
(p[3]&p[2]&p[1]&p[0]&c[0])|(p[3]&p[2]&p[1]&g[0])|(p[3]&p[2]&g[1])|(p[3]&g[2])|g[3];
```

```
    assign Cout=c[4];

    assign S[0]=p[0]^c[0];
    assign S[1]=p[1]^c[1];
    assign S[2]=p[2]^c[2];
    assign S[3]=p[3]^c[3];

endmodule
```

Test Bench Code:

```
module cla_4bit_test;

    // Inputs
    reg [3:0] a;
    reg [3:0] b;
    reg Cin;

    // Outputs
    wire [3:0] S;
    wire Cout;
    reg [4:0]check;

    // Instantiate the Unit Under Test (UUT)
    CLA_4bit uut (
        .a(a),
        .b(b),
        .Cin(Cin),
        .S(S),
        .Cout(Cout)
    );
endmodule
```

```
initial repeat(20) begin
    // Initialize Inputs
    a = $random;
    b = $random;
    Cin = $random;
    check=a+b+Cin;

    // Wait 100 ns for global reset to finish
    #10 $display($time,"%d+%d+%d=%d(%d)",a,b,Cin,{ Cout,S },check);

    // Add stimulus here

end

endmodule
```

Result:

Successfully designed, implemented and tested 4 Bit Carry Look Ahead Adder circuit using Xilinx ISE Tool.

Device utilization summary:

Selected Device : 3s500efg320-4

Number of Slices:	4 out of 4656	0%
Number of 4 input LUTs:	8 out of 9312	0%
Number of IOs:	14	
Number of bonded IOBs:	14 out of 232	6%

Timing Summary:

Speed Grade: -4

Minimum period: No path found

Minimum input arrival time before clock: No path found

Maximum output required time after clock: No path found

Maximum combinational path delay: 9.882ns

