

## Experiment 1

## VLSI

## 4 Bit Ripple Carry Adder


Shashank Sharma

15BEE0270

L47+L48

**Objective:**

To design, implement and test 4 Bit Ripple Carry Adder circuit using Xilinx ISE Tool.

 **Circuit Diagram:**

## Design code:

```
module Ripple_Counter(  
    input [3:0]a,b,  
    input Cin,  
    output [3:0]S,  
    output Cout  
);  
wire c1,c2,c3;  
fa_df fa1(a[0],b[0],Cin,S[0],c1);  
fa_df fa2(a[1],b[1],c1,S[1],c2);  
fa_df fa3(a[2],b[2],c2,S[2],c3);  
fa_df fa4(a[3],b[3],c3,S[3],Cout);  
endmodule
```

## Test Bench Code

```
module Ripple_Counter_test;  
    // Inputs  
    reg [3:0] a;  
    reg [3:0] b;  
    reg Cin;  
  
    // Outputs  
    wire [3:0] S;  
    wire Cout;  
    reg [4:0] check;
```

```
// Instantiate the Unit Under Test (UUT)

    Ripple_Counter uut (
        .a(a),
        .b(b),
        .Cin(Cin),
        .S(S),
        .Cout(Cout)
    );

    initial repeat(20) begin
        // Initialize Inputs
        a = $random;
        b = $random;
        Cin = $random;
        check=a+b+Cin;

        // Wait 100 ns for global reset to finish
        #10 $display($time, " %d+%d+%d=%d(%d)", a,b,Cin,{Cout,S},check)
    end

endmodule
```

## Result

Successfully designed, implemented and tested 4 Bit Ripple Carry Adder circuit using Xilinx ISE Tool.

Device utilization summary:

-----

Selected Device : 3s500efg320-4

Number of Slices:	4 out of 4656	0%
Number of 4 input LUTs:	8 out of 9312	0%
Number of IOs:	14	
Number of bonded IOBs:	14 out of 232	6%

Timing Summary:

-----

Speed Grade: -4

Minimum period: No path found

Minimum input arrival time before clock: No path found

Maximum output required time after clock: No path found

Maximum combinational path delay: 9.926ns

